

CHRISTIAN SOCIAL SERVICES COMMISSION (CSSC)
NORTHERN ZONE JOINT EXAMINATIONS SYNDICATE (NZ-JES)



FORM FOUR PRE – NATIONAL EXAMINATION AUGUST 2025

PHYSICS 2A
MARKING SCHEME

1. (i) Table of results

Length L(cm)	10	20	30	40	50
Number of oscillations (n)	20	20	20	20	20
Time t (sec)	14	19	24	27	30
$t^2(s^2)$	196	361	576	729	900

02markseachcolumnntotalmarks10

(ii) Graph draw on graphpaper.

(iii) From the graph, slope = $\frac{\Delta t^2 L S^2}{\Delta L cm}$ **01mark**

$$= \frac{780-220}{45-10}$$

00 ½ marks

$$= 16 S^2/m = 1600 S^2/m$$

01 mark

(iv) From $t^2 = \frac{4\pi^2 n^2 L}{z} + C, m = \frac{4\pi^2 n^2 L}{z}, z = \frac{4\pi^2 n^2 L}{m}, z = \frac{4\pi^2 \times 20^2}{1620} = 9.8696 m/s^2$ **01mark**

$$Z = t^2 \frac{4\pi^2 \times 20^2}{1620} = 9.8696 m/s^2$$

[02marks]

(v) Significance of z

(i) It help to pull everything towards the centre of the earth.

(ii) It help people to work.

(iii) It help to know the depth of the ocean and height of the mountain. **Only one point (1mark)**

(vi) The aim of experiment is to determine acceleration due to gravity. **[01mark]**

THE GRAPH OF $t^2(s^2)$ AGAINST LENGTH $L(cm)$


Scale

Vertical scale:

1cm represents 120 sec

Horizontal scale:

1cm represents 10cm

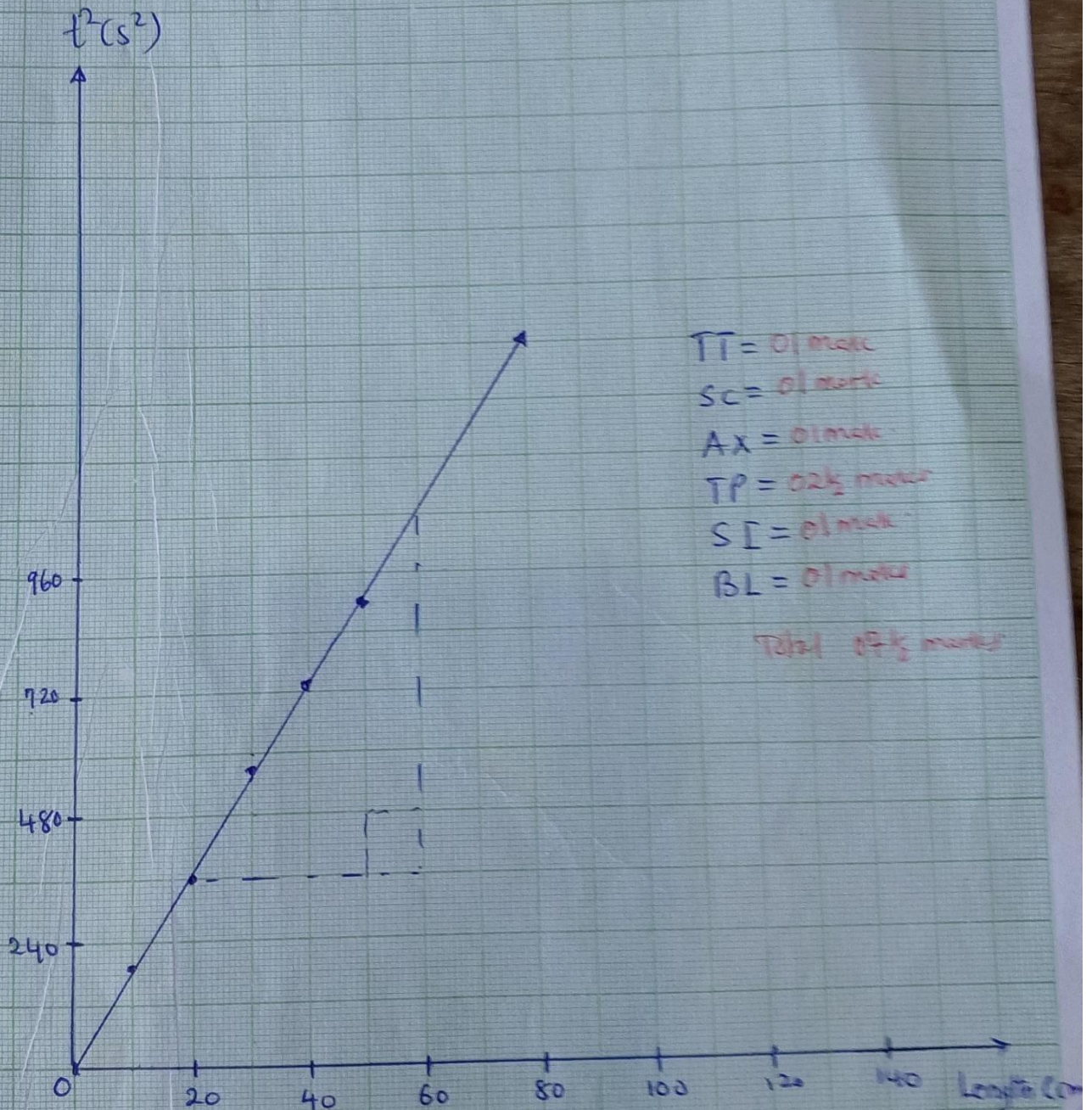

TT = 0.1 mark

SC = 0.1 mark

AX = 0.1 mark

TP = 0.25 mark

SI = 0.1 mark

BL = 0.1 mark

Total 0.75 marks


(1 cm = 1 cm squares of 10mm x 10mm)

2. (a) table of results

Resistance R (ohm)	V (VOLT)	A (SI)
1	0.98 (0.55– 1.4)	1.00
2	1.20	0.60
3	1.28	0.43
4	1.30	0.33
5	1.35	0.27

@row 1 mark = (05 marks)

(b) The circuit diagram

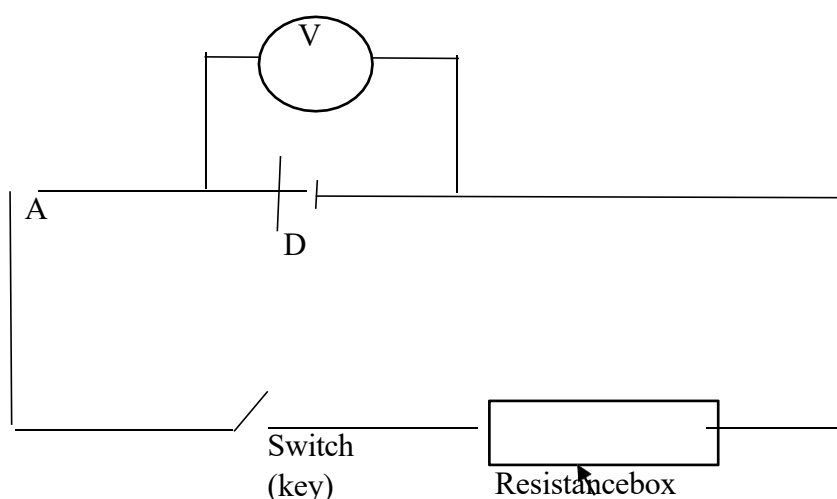

[02marks]

(c) From

$$\begin{aligned}
 E &= I(R+r) \\
 E &= IR + Ir \\
 E &= V + Ir \\
 V &= E - Ir
 \end{aligned}$$

[01 ½marks]

(c)(i) From the graph E is the vertical intercept which is $E = 1.48\text{V}$. **03marks**

(ii) Internal resistance = -Slope of the graph **01mark**

$$\begin{aligned}
 &= -\frac{\Delta V(V)}{\Delta I(A)} \\
 &= \frac{-(1.3-0.4)\text{V}}{(0.375-2.25)\text{A}}
 \end{aligned}$$

$$= \frac{0.9}{-1.875} \text{ ohm} \quad \text{(01mark)}$$

$$= 0.48 \text{ ohm} \quad 0.45-0.55 \quad \text{(01mark)}$$

(iii) The maximum current the cell can deliver to the circuit is the horizontal axis intercept is $I = 3.075\text{A}$ (2.22-3.33) **(03marks)**

A GRAPH OF V(Volts) AGAINST I(Amps)

SCALE;
Horizontal scale:
1cm represents 0.25
Vertical scale:
1cm represents 0.1V.

